




SOLVING THE RESISTOR LADDER PROBLEM USING MATRIX MATH

Wissam Razouki
CSE 3802





INTRODUCTION



The Problem

The equations for solving for the voltages at each node for nodes 1 through N in the resistor ladder are given as:

$$\begin{aligned} \text{Node 1: } I_s &= \frac{V_1 - V_2}{R_{s1}} \text{ or } I_s = (V_1 - V_2) G_{s1} \\ \text{Node 2: } \frac{V_1 - V_2}{R_{s1}} &= \frac{V_2 - V_3}{R_{s2}} + \frac{V_2}{R_{g1}} \text{ or } (V_1 - V_2) G_{s1} = (V_2 - V_3) G_{s2} + V_2 G_{g1} \\ \text{Node 3: } \frac{V_2 - V_3}{R_{s2}} &= \frac{V_3 - V_4}{R_{s3}} + \frac{V_3}{R_{g2}} \text{ or } (V_2 - V_3) G_{s2} = (V_3 - V_4) G_{s3} + V_3 G_{g2} \\ &\dots \\ \text{Node } N: \frac{V_{N-1} - V_N}{R_{sN-1}} &= \frac{V_N}{R_{gN-1}} \text{ or } (V_{N-1} - V_N) G_{sN-1} = V_N G_{gN-1} \end{aligned}$$

Where the current source I_s and the resistor values R_s and R_g are known, and $G = \frac{1}{R}$.

In order to convert this linear system to matrix form, we must first rewrite the equations in the form $GV = I$.

Rewritten Equations

The above system can be rewritten as:

$$G_{s1}V_1 - G_{s1}V_2 = I_s$$

$$G_{s1}V_1 - (G_{s1} + G_{s2} + G_{g1})V_2 + G_{s2}V_3 = 0$$

$$G_{s2}V_2 - (G_{s2} + G_{s3} + G_{g2})V_3 + G_{s3}V_4 = 0$$

\vdots

$$G_{sN-1}V_{N-1} - (G_{sN-1} + G_{gN-1})V_N = 0$$

This system can easily be converted to the matrix form $\mathbf{Ax} = \mathbf{b}$ (or $\mathbf{GV} = \mathbf{I}$).

Resultant Matrix Form

$$\begin{array}{c}
 \begin{matrix} N \\ \left\{ \begin{array}{c} \begin{array}{ccccccc} G_{s1} & -G_{s1} & 0 & 0 & \dots & 0 \\ G_{s1} & -(G_{s1}+G_{s2}+G_{g1}) & G_{s2} & 0 & 0 & \dots & 0 \\ 0 & G_{s2} & -(G_{s2}+G_{s3}+G_{g2}) & G_{s3} & \dots & 0 \\ \vdots & \vdots & \vdots & \vdots & \ddots & \vdots & \vdots \\ 0 & \dots & 0 & 0 & G_{sN-1} & -(G_{sN-1}+G_{gN-1}) \end{array} \end{array} \right\} \end{matrix} \\
 \\
 \times \begin{pmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{pmatrix} = \begin{pmatrix} I_s \\ 0 \\ 0 \\ \vdots \\ 0 \end{pmatrix}
 \end{array}$$

Now that we have matrix **A** and vector **b**, we can implement the solution methods for **x**.

Methods Used

Reference method:

- Exact solution using MATLAB

Experimental method:

- Jacobi iteration



METHODS

The Exact Solution

MATLAB provides a direct solution to \mathbf{x} given \mathbf{A} and \mathbf{b} . The command for this is:
 $\mathbf{x} = \mathbf{A} \backslash \mathbf{b}.$

We can use this to compare to our experimental method.

Jacobi Method

- Solves for \mathbf{x} iteratively
- Requires computation of the diagonal \mathbf{D} and remainder \mathbf{R} of \mathbf{A}
- Only works on square matrices that are strictly diagonally dominant
- The spectral radius of the iteration matrix must be less than 1 to guarantee convergence. This is defined as

$$\rho(D^{-1}R) = \max(|\lambda_1|, \dots, |\lambda_N|)$$

I chose this method because MATLAB provides built-in functions for obtaining these parameters. Also, the system satisfies all the necessary conditions.

$$A = \begin{bmatrix} a_{11} & a_{12} & \cdots & a_{1n} \\ a_{21} & a_{22} & \cdots & a_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ a_{n1} & a_{n2} & \cdots & a_{nn} \end{bmatrix}, \quad \mathbf{x} = \begin{bmatrix} x_1 \\ x_2 \\ \vdots \\ x_n \end{bmatrix}, \quad \mathbf{b} = \begin{bmatrix} b_1 \\ b_2 \\ \vdots \\ b_n \end{bmatrix}.$$

$$A = D + R \quad \text{where} \quad D = \begin{bmatrix} a_{11} & 0 & \cdots & 0 \\ 0 & a_{22} & \cdots & 0 \\ \vdots & \vdots & \ddots & \vdots \\ 0 & 0 & \cdots & a_{nn} \end{bmatrix} \quad \text{and} \quad R = \begin{bmatrix} 0 & a_{12} & \cdots & a_{1n} \\ a_{21} & 0 & \cdots & a_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ a_{n1} & a_{n2} & \cdots & 0 \end{bmatrix}.$$

From Wikipedia

Method Verification


MATLAB provides tools for generating random values for matrices and vectors.

Setting \mathbf{A} to a random $N \times N$ matrix and \mathbf{b} to a random column vector of size N , we can solve for \mathbf{x} using the Jacobi method and then compare this result to the exact solution.

This can be run continuously until a system that meets the spectral radius requirements is found.

I set up the Jacobi method to iterate 500 times for high accuracy.

The absolute error ($|\textit{reference} - \textit{experimental}|$) for a particular system with $N = 4$ is plotted below. Since the error is on a magnitude of 10^{-16} , I can conclude that my implementation is correct.

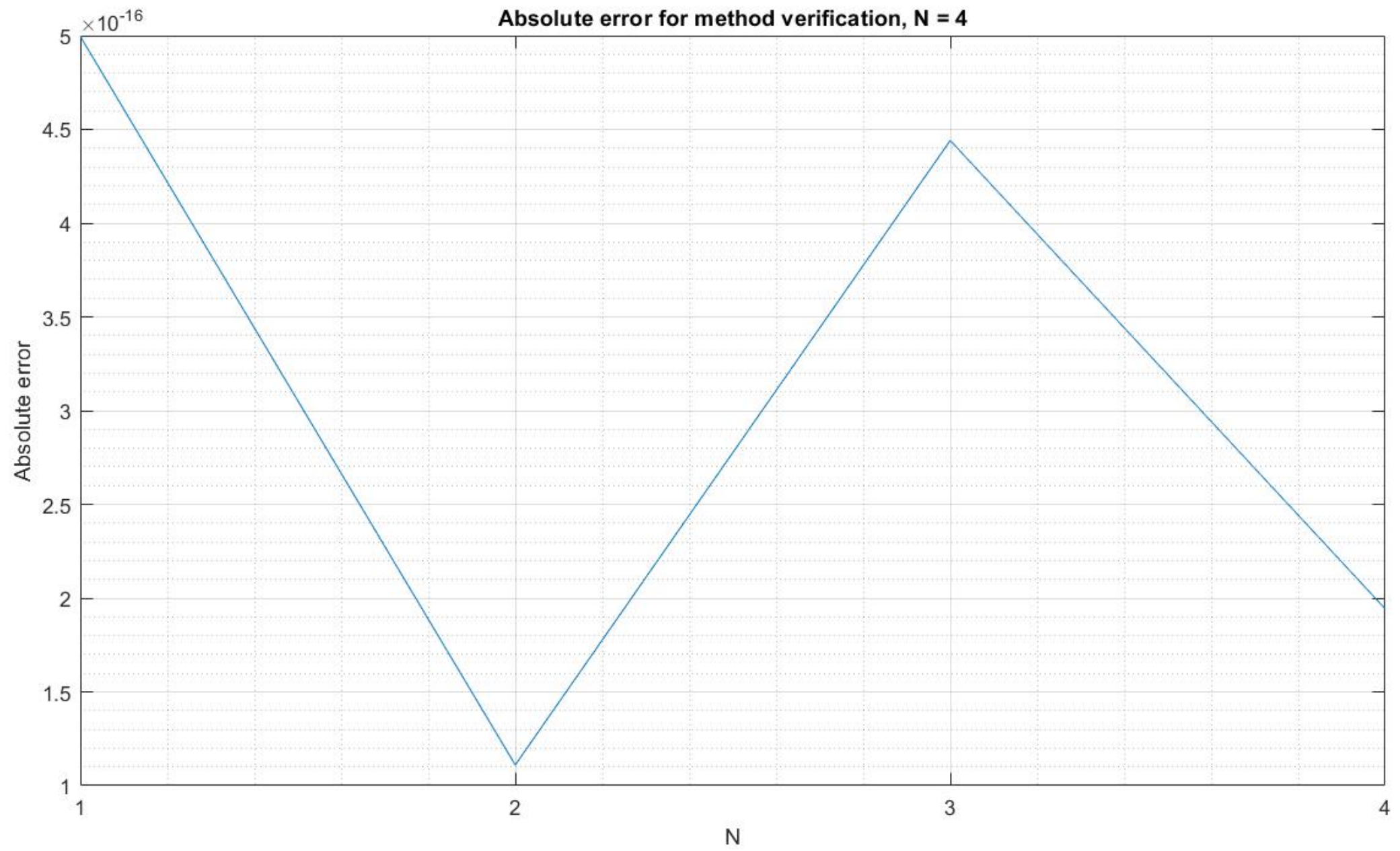



SOLUTIONS: CASE 1 AND CASE 2




Case 1

The Jacobi method was set to iterate 500 times, which provided results that were almost exactly equal to the actual solutions.

The solutions for V_1, \dots, V_{10} are given here.

The absolute error is plotted below.

Voltage (V)
869.4368
69.4368
8.3104
1.3392
0.2659
0.0641
0.0217
0.0124
0.0105
0.0102

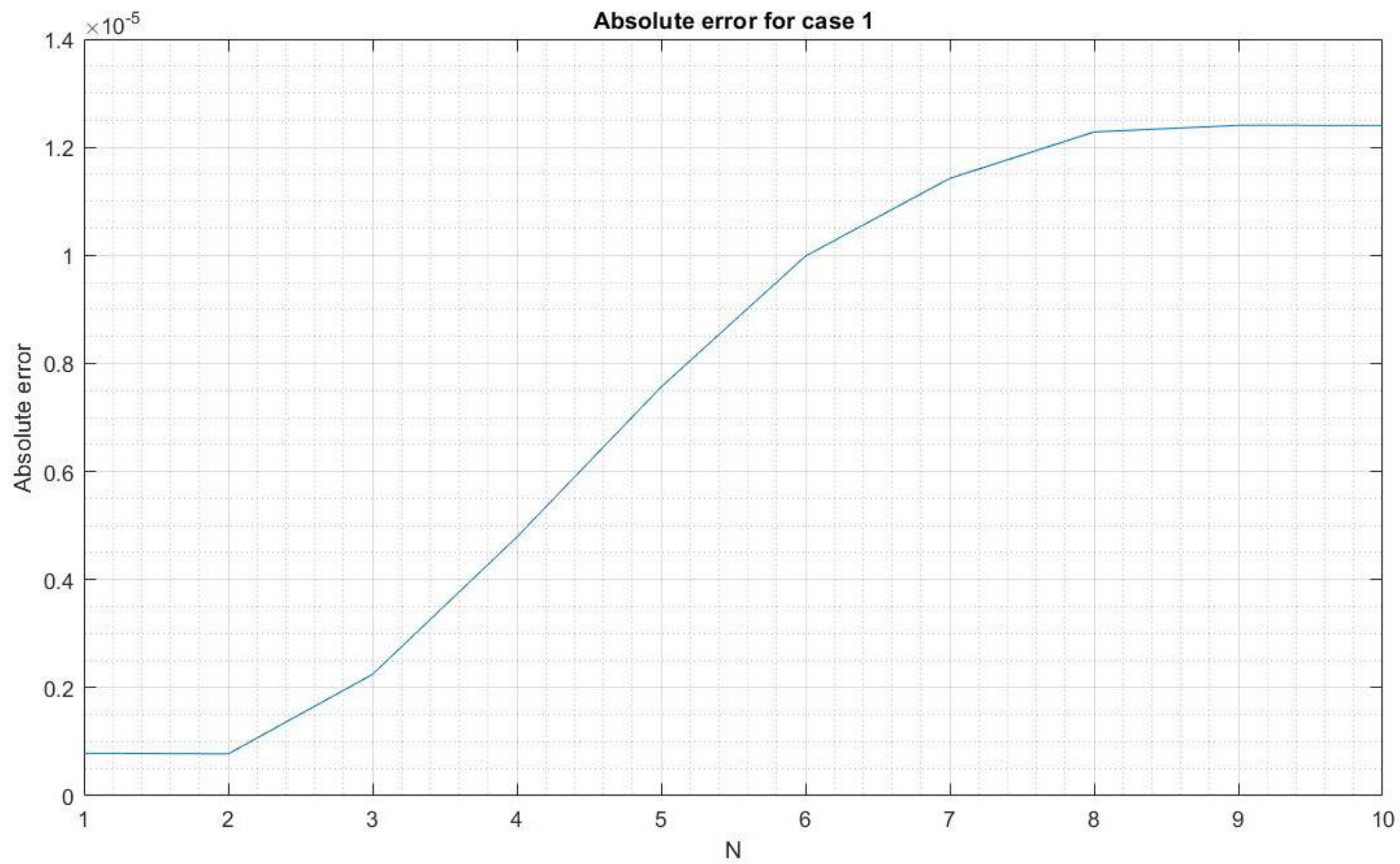

Case 2

The golden ratio is approximately:

$$\frac{1 + \sqrt{5}}{2} = 1.618$$


I set all resistance values to $R = 1 \Omega$ for simplicity.

After some experimentation, I found that a value of $N = 8$ provided a close enough value to the golden ratio.

The solutions for V_1, \dots, V_8 are given here.

The absolute error is plotted below.

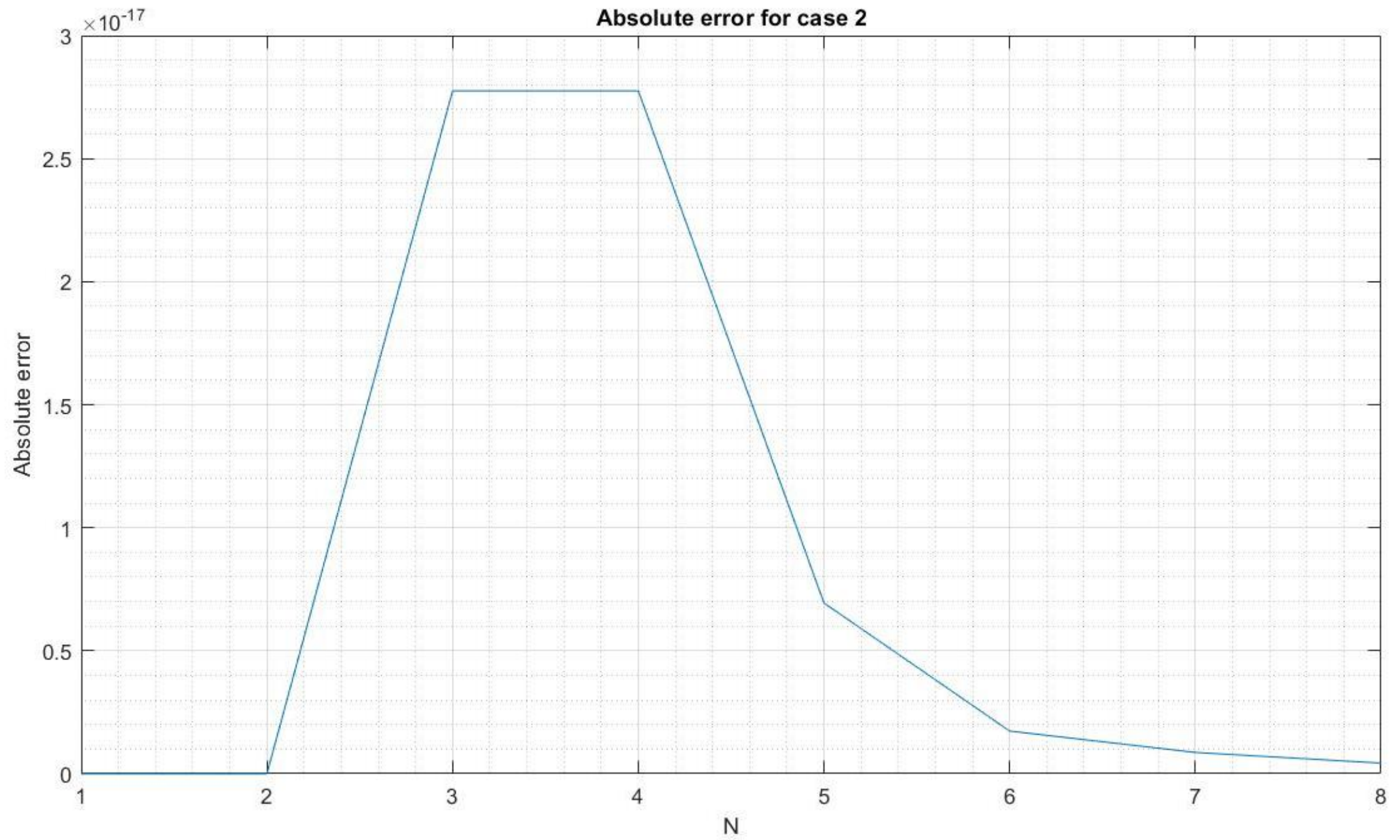Voltage (V)
1.6180
0.6180
0.2361
0.0902
0.0345
0.0133
0.0053
0.0027





CONCLUSIONS



Analysis and Conclusions

From these results, we can see that the Jacobi method provides very accurate solutions when it is set up to iterate many times.

- However, the conditions (square matrix, spectral radius, etc.) are strict. If they are not met, the results could be very inaccurate or the method could fail entirely
- Because this particular problem satisfies all conditions, no errors were met
- But there are many conditions where my code fails to solve the problem. Given a system with either:
 - *A non-square matrix*
 - *An iteration matrix with a spectral radius of greater than 1*
 - *A matrix that is not strictly diagonally dominant*

the Jacobi method could fail to give an accurate result